

# EDW Assignment - 1: 7-Segment Display Logic Mapper

MAHIB - 2023UEC2569

January 2025

## Objective

The objective of this assignment was to design a schematic involving a 4-input DIP switch, a custom logic mapper, and a 7-segment display. The project required creating Boolean expressions for the custom logic mapper and connecting the outputs to the respective inputs of a 7-segment display.

## Schematic Overview

The schematic consists of four input signals labeled  $A$ ,  $B$ ,  $C$ , and  $D$ . These inputs are connected to a 4-input DIP switch, which allows the user to toggle between different logic states. The outputs from the DIP switch are then fed into a custom logic mapper, which calculates the values for seven output signals:  $a$ ,  $b$ ,  $c$ ,  $d$ ,  $e$ ,  $f$ , and  $g$ . These outputs are connected to the respective inputs of the 7-segment display.

## Logic Mapper

The logic mapper consists of the following Boolean equations for the seven outputs:

$$a = B'D' + BC + AD' + A'C + AB'C' + A'BD$$

$$b = B'D' + B'C' + A'CD + AC'D + A'C'D'$$

$$c = AB' + C'D + A'B + A'D + B'C'$$

$$d = BCD' + ABC' + B'C'D' + BC'D + A'B'C' + B'CD$$

$$e = B'D' + CD' + AB + AC$$

$$f = AB' + BD' + AC + C'D' + A'BC'$$


$$g = CD' + AB' + B'C + AD + A'BC'$$

## 7-Segment Display


The outputs from the logic mapper are connected to the respective red inputs of a 7-segment display. The common anode input of the display is connected to  $V_{cc}$  (5V), with a 220-ohm resistor in series to maintain the required 2V potential difference across the LEDs in the display.
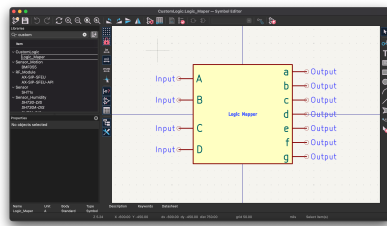
## Schematic and Custom Symbols


Below are the images for the schematic design and the custom symbols used in the project. Each image is displayed as a subfigure.




(a) Logic Mapper Custom Symbol

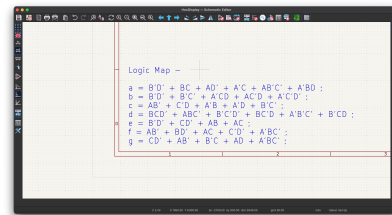

(b) Logic Mapper Equations

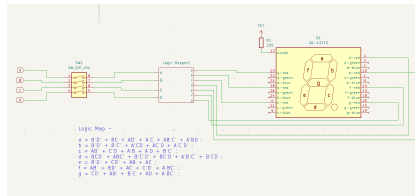

(c) Schematic

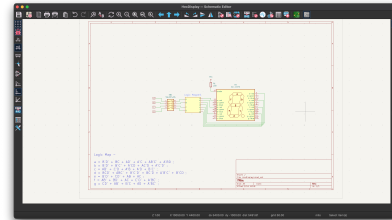

(d) Full Schematic

Figure 1: Schematic and Custom Symbols

## Conclusion

This assignment allowed me to design a complex logic circuit with multiple inputs and outputs, and connect them to a 7-segment display to visualize the results. The custom logic mapper was designed using Boolean expressions and the 7-segment display was wired with the appropriate components to display the output in a readable format.